

COMP1011

(2)

- (c) (i) Discuss different types of programming languages. 6+2+2
- (ii) What is Gray code? Convert $(01001)_2$ to its equivalent Gray code. 5+5
- (d) Write short notes on *any two*:
- (i) Comparator circuit (2 bit)
 - (ii) Master slave J-K Flip Flop
 - (iii) Binary Coded Decimal (BCD)
 - (iv) Johnson's counter
-

3 Yr. Degree/4 Yr. Honours 1st Semester Examination, 2024 (CCFUP)

Subject : Computer Science

Course: COMP1011 (MAJOR)

(Computer Fundamentals and Digital Logic)

Time: 2 Hours

Full Marks: 40

*The figures in the margin indicate full marks.**Candidates are required to give their answers in their own words as far as practicable.*

1. Answer any five questions:

2×5=10

- (a) What is Mini Computer?
- (b) Convert $(745)_8$ to Hexadecimal Number System.
- (c) Why NOR Gate is called Universal Gate?
- (d) Write the difference between Minterm and Maxterm.
- (e) Write two disadvantages of K-Map.
- (f) What is weighted code?
- (g) What do you mean by sequential circuit?
- (h) What is race around condition?

2. Answer any two questions:

5×2=10

- (a) Simplify the following Boolean expression using K-map.
 $f(A, B, C) = \sum m(1, 3, 5, 6, 7).$
- (b) (i) Design a full adder circuit with the help of half adders and logic gate.
 (ii) What is BCD Adder?
- (c) (i) Construct a 16×1 MUX using 8×1 MUX and logic gates.
 (ii) What do you mean by parity bit?
- (d) Discuss a single bit error detection and corrections code.

3+2

4+1

3. Answer any two questions:

10×2=20

- (a) Design mod 7 counter using T Flip Flop.
- (b) (i) Explain clocked SR Flip Flop using NAND Gate and using NOR Gate.
 (ii) What is Excitation table?

10

8+2