

3 Yr. Degree/4 Yr. Honours 1st Semester Examination, 2023 (CCFUP)

Subject : Computer Science

Course: COMP1011 (MAJOR)

(Computer Fundamental & Digital Logic)

Time: 2 Hours

Full Marks: 40

The figures in the right hand margin indicate full marks.

*Candidates are required to give their answers in their own words
as far as practicable.*

1. Answer any five of the following questions: 2×5=10

- (a) What is Flow Chart?
- (b) Define Pseudo Code.
- (c) State De Morgan's Theorem.
- (d) Why NAND Gate is called Universal Gate?
- (e) Define Latch.
- (f) What do you mean by sequential circuit?
- (g) Write the difference between Parity Generator and Parity Checker.
- (h) What is Decision Table?

2. Answer any two of the following questions: 5×2=10

- (a) What do you mean by Computer Programming Language? Discuss in brief Machine and Assembly Language. 1+2+2
- (b) What is Gray Code? Write steps to convert Binary to Gray Code. Convert $(100110)_2$ to Gray Code. 2+2+1
- (c) Discuss S-R and J-K Flip Flop with diagram and Truth Table. 2.5+2.5
- (d) Design a four bit shift register with parallel load. 5

3. Answer any two of the following questions: 10×2=20

- (a) (i) Simplify the following Boolean expression using 4 variable K-Map.

$$f(A,B,C,D) = \sum m(2,3,6,7,8,10,13,15)$$

- (ii) Write the drawbacks of K-map. 8+2

- (b) What do you mean by Decoder? Design a 4×16 decoder using 3×8 decoders and any additional logic gates. 2+8
- (c) What is the difference between Synchronous and Asynchronous Counter? Design a 3 bit Asynchronous Up / Down Counter. 2+8
- (d) Write shorts note on *any two* : 5×2=10
- (i) ASCII
 - (ii) Single Error Detecting and Correcting Codes
 - (iii) Master-Slave J-K Flip Flop
 - (iv) Ripple Counter
-